




Problem 1

1. Design a two input, two output circuit that yields the sum and difference of inputs, $V_{\text{sum}} = V_1 + V_2$ and $V_{\text{diff}} = V_1 - V_2$. Try minimizing the component count.

Problem 2



2. Determine $R_{eq} = V_{in}/I_{in}$ of the circuit shown in below Figure.

(b) Given $V_{in} = 2V$, $R_x = R_1 = 1k\Omega$, $R_f = 2k\Omega$. Obtain R_{eq} .

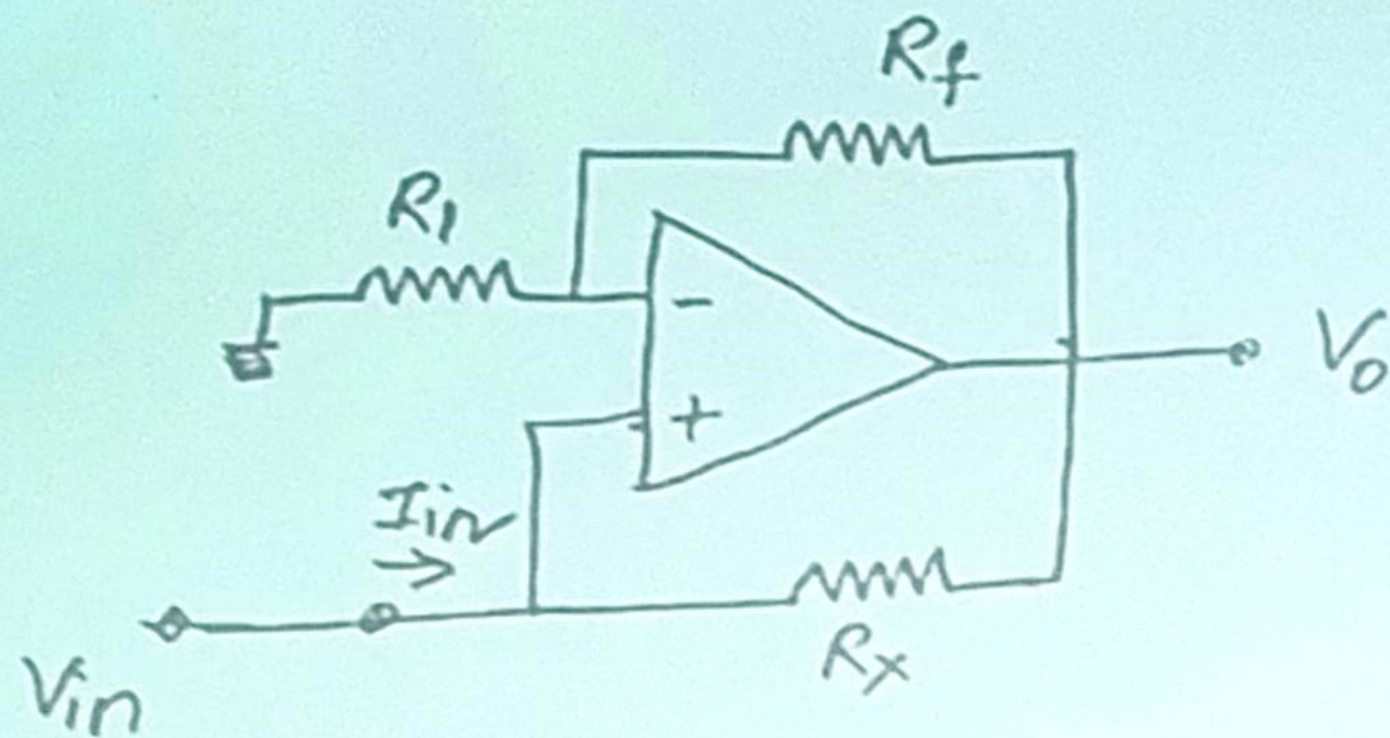

Problem 3

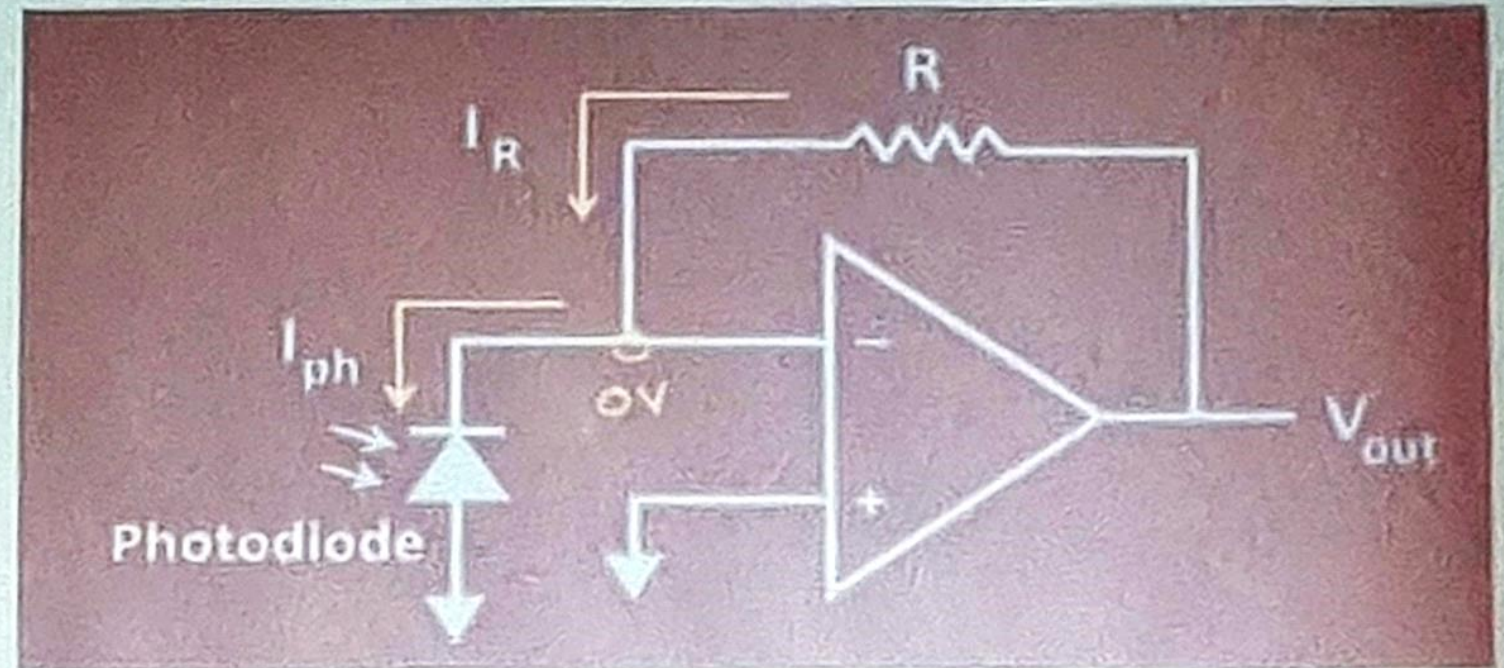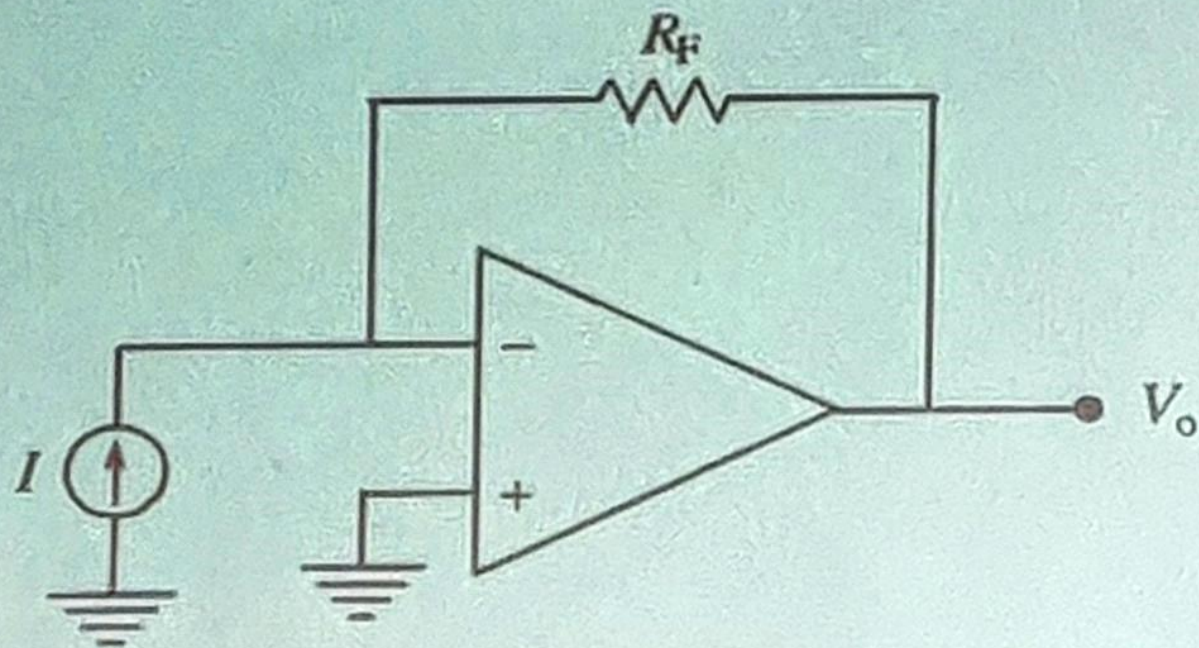
3. Design a circuit to convert 4mA to 20 mA input current to 0V to 8 V output voltage. The reference direction of input current is from ground to circuit
(Transimpedance Amplifier – CCVS – Voltage Shunt Feedback)



Example : Current to Voltage Converter



Problem 4

4. If $v_1 = 1V$ and $v_2 = 0.5V$, find V_o

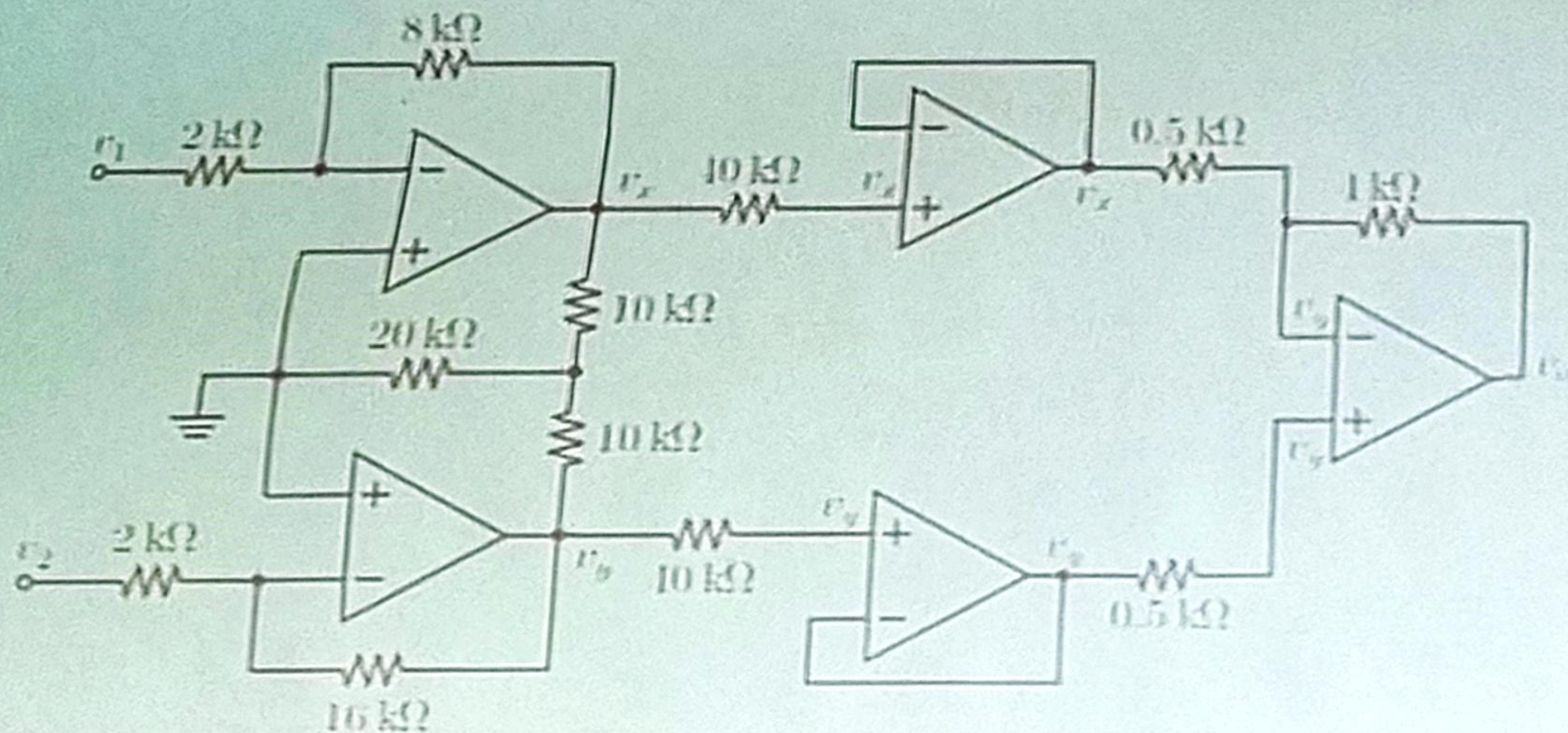


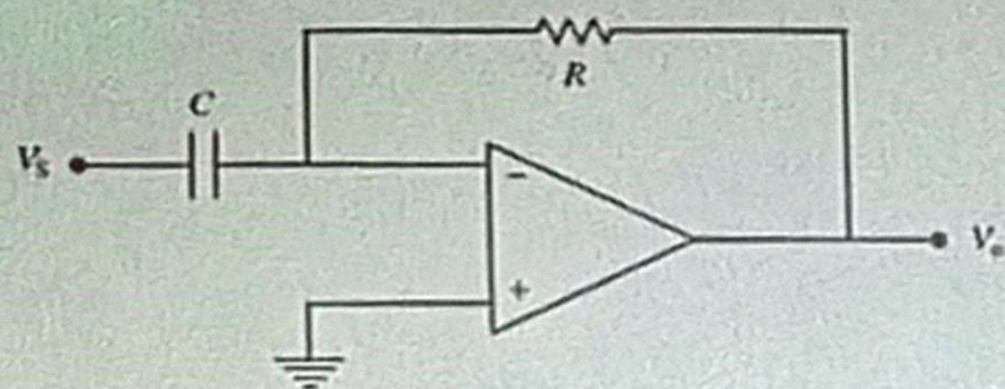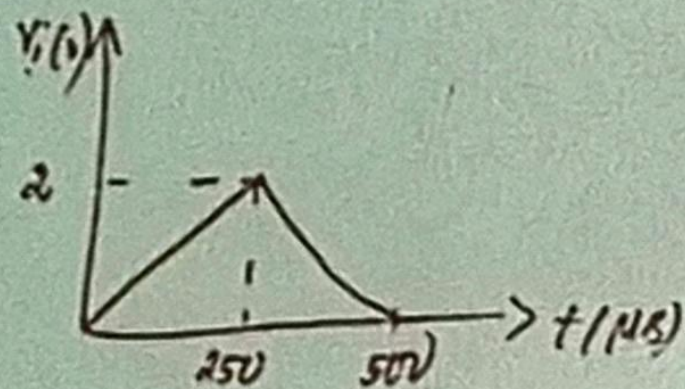Problem 5

The input to the differentiator circuit is shown in fig. Find the output V_o if $R_f = 2 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$.



5. Solution

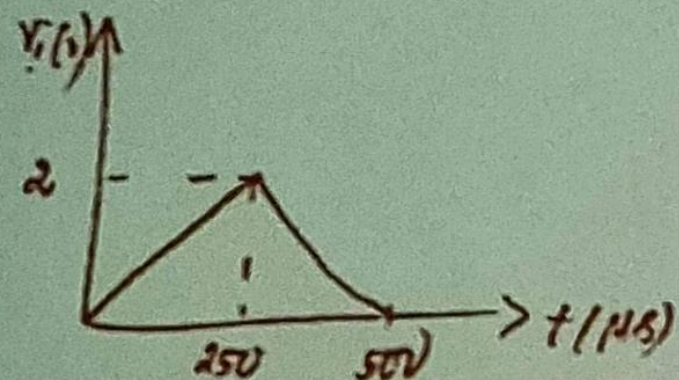

for $0 < t < 250 \text{ } \mu\text{s}$

$$V_i(t) = 8000t$$

$$\left. \begin{array}{l} \dot{V}_i(t) = 0 \text{ at } t=0 \\ \dot{V}_i(t) = 2 \text{ at } t=250 \text{ } \mu\text{s} \end{array} \right\}$$

The output of differentiator $V_o = -R_f C_1 \frac{d}{dt} V_i(t)$

$$\begin{aligned} V_o &= -2 \times 10^3 \times 0.1 \times 10^{-6} \frac{d}{dt} (8000t) \\ &= -1.6 \text{ V} \end{aligned}$$

Similarly, for $250 \text{ } \mu\text{s} < t < 500 \text{ } \mu\text{s}$

$$V_o = 1.6 \text{ V}$$